

2nd communication

Logic 2 project report

Logic_project_70

Super Register

Team members

Engy Ashraf 70

Andrew Morcos 71

Mina Nabil 296

Youstina Abd Elmassih 325

Super register project

1st Steps

We asked to design super register that performs eight operations:

- Load data
- Shift data to left
- Shift data to right
- Rotate data to left
- Rotate data to right
- Store data (store its state)
- Count up
- Count down

And to get first output of these operations according to control input -consists of three bits- and second output according to the first output.

So, we thought of this project in behavioral way, this by creating an entity containing all these ports:

- Data_in (8 bits vector input).
- Control (3 bits vector input).
- Sh_r, Sh_l, clk (1 bit input).
- Data_out1 (8 bits vector output).
- Data_out2 (1 bit vector output).


Then creating its architecture which contains:

- Process.


In the process we wrote our algorithm which depends on using case statements and we switched between statements using the control input, so we converted 8 operations into 8 case statements, in each case we wrote the code which performs this case (operation) and as process is sensitive to CLK and control so at each rising edge the process checks which case should be done.

2nd schematic

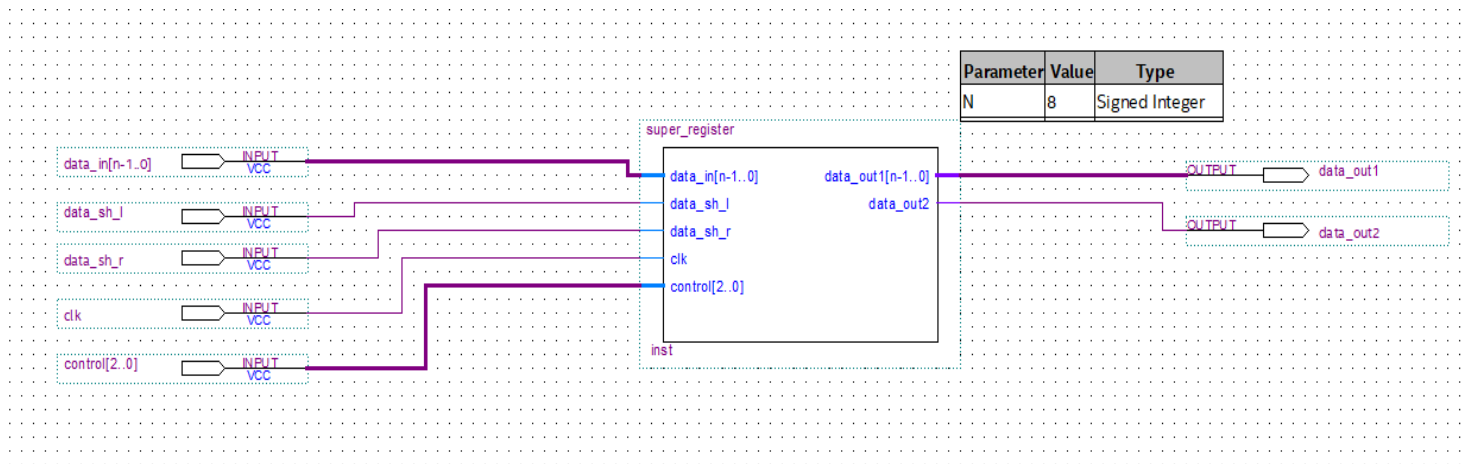
By using QUARTUS program we converted our code into this block diagram



which consists of three main parts:

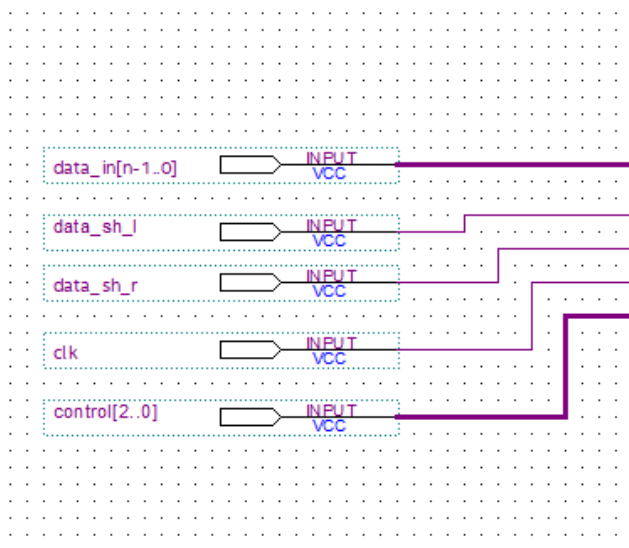


part1(inputs)

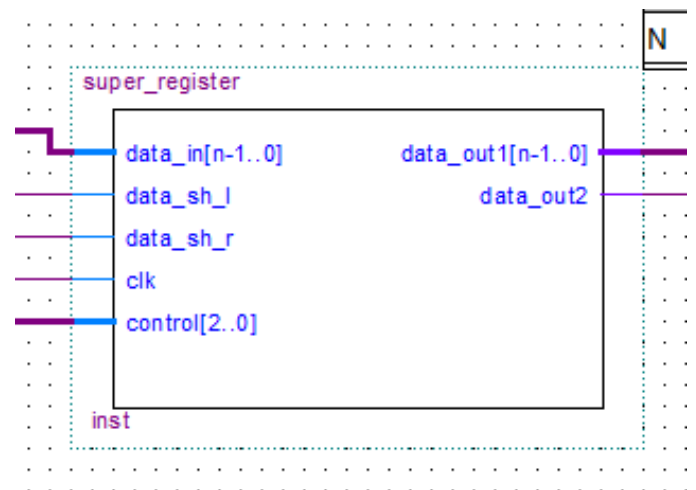


Part2(our operational block)

Parameter	Value	Type
N	8	Signed Integer

 

Part3(outputs)

SUPER REGISTER

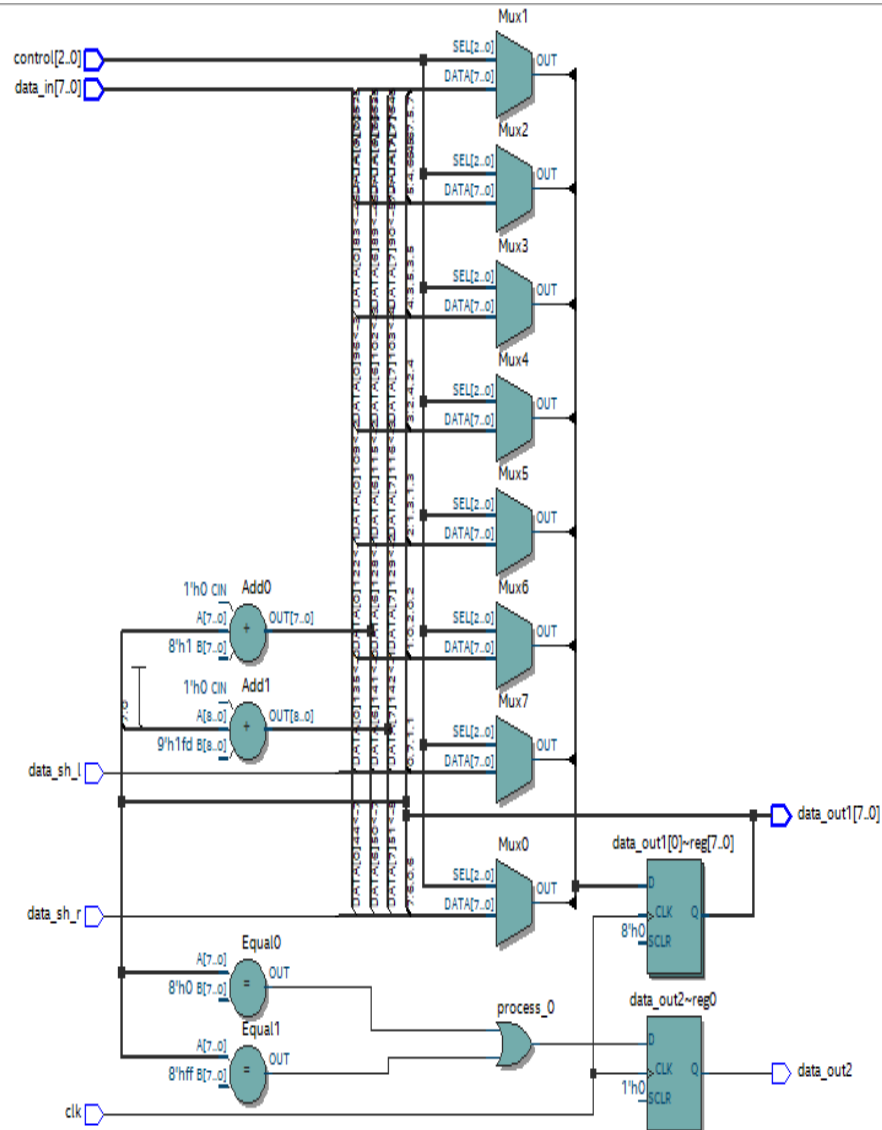

3rd VHDL code

Text Editor - C:/intelFPGA_lite/17.1/super_register - super_register - [super_reg.vhd]

File Edit View Project Processing Tools Window Help

```

1  library ieee;
2  use ieee.std_logic_1164.all;
3  use ieee.std_logic_unsigned.all;
4
5  entity super_register is
6      generic ( N : integer := 8);
7      port( data_in : in std_logic_vector(N-1 downto 0);
8            data_sh_l, data_sh_r, clk : in std_logic;
9            control : in std_logic_vector(2 downto 0);
10           data_out1: buffer std_logic_vector(N-1 downto 0);
11           data_out2: out std_logic);
12  end super_register;
13
14  architecture behavoir of super_register is
15  begin
16      process(control, clk)
17          variable tmp : std_logic;
18          variable zero_all : std_logic_vector(N-1 downto 0) := (others => '0') ;
19          variable one_all : std_logic_vector(N-1 downto 0) := (others => '1');
20      begin
21          if clk'event and clk = '1' then
22              case control is
23                  when "000" => --load new data
24                      data_out1 <= data_in;
25                  when "001" => -- right shift
26                      l_shift: for i in 0 to N-2 loop
27                          data_out1(i) <= data_out1(i+1);
28                      end loop;
29                      data_out1(N-1) <= data_sh_r;
30                  when "010" => -- left shift
31                      r_shift: for i in N-1 downto 1 loop
32                          data_out1(i) <= data_out1(i-1);
33                      end loop;
34                      data_out1(0) <= data_sh_l;
35                  when "011" => -- left rotate
36                      tmp := data_out1(0);
37                      l_rotate: for i in 0 to N-2 loop
38                          data_out1(i) <= data_out1(i+1);
39                      end loop;
40                      data_out1(N-1) <= tmp;
41                  when "100" => -- right rotate
42                      tmp := data_out1(N-1);
43                      r_rotate: for i in N-1 downto 1 loop
44                          data_out1(i) <= data_out1(i-1);
45                      end loop;
46                      data_out1(0) <= tmp;
47                  when "101" => --store present state
48                      data_out1 <= data_out1;
49                  when "110" => -- count up
50                      data_out1 <= data_out1 + 1 ;
51                  when others => -- count down
52                      data_out1 <= data_out1 - 1 ;
53              end case;
54
55              if(data_out1 = zero_all or data_out1 = one_all) then
56                  data_out2 <= '1';
57              else
58                  data_out2 <= '0';
59              end if;
60
61          end if;
62      end process;
63  end behavoir;
64
65
66
67

```

This is libraries declaration, we use here three libraries

- IEEE
- IEEE.std_logic_1164.all.
- IEEE.std_logic_unsigned.all (we use this to perform adding on a vector)


1) Entity declaration

- Generic (It gives us ability to extend our register to more than 8 bits)
- Ports


2) Architecture

- Process
 - a) Variable
 - Tmp (we use it to save the last or first bit in rotating mode)
 - b) constants
 - Zero_all (we use it to compare between it and data_out having same size)
 - One_all (we use it to compare between it and data_out having same size)
 - c) Process body
 - Case statements
 - i) Loading data
 - ii) Right shifting using for loop to pass each bit to its right adjacent one
 - iii) Left shifting using for loop to pass each bit to its left adjacent one
 - iv) Left rotating using for loop like left shifting but without inserting external bit
 - v) Right rotating using for loop like right shifting but without inserting external bit
 - vi) Storing data by passing output again to the output using buffer
 - vii) Counting up by simply adding one to the output state
 - viii) Counting down by simply subtracting one from the output state
 - If statement
 - Used to assign to the second output 1 if the first output is 11111111 or 00000000 else it assigns it with 0


4th simulations

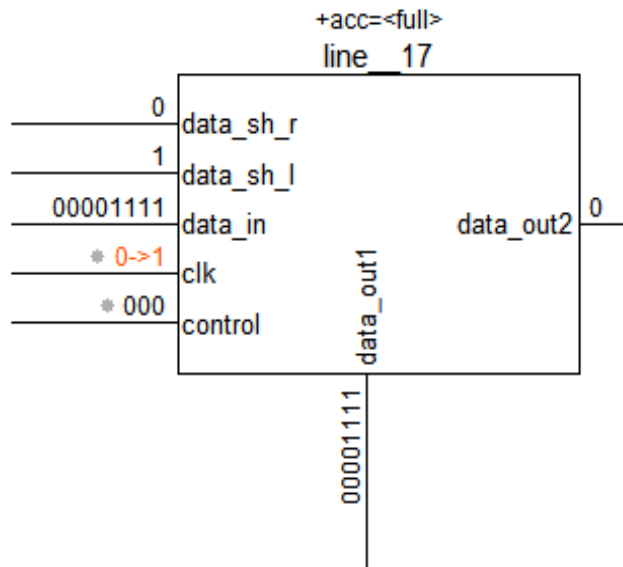


Insert data

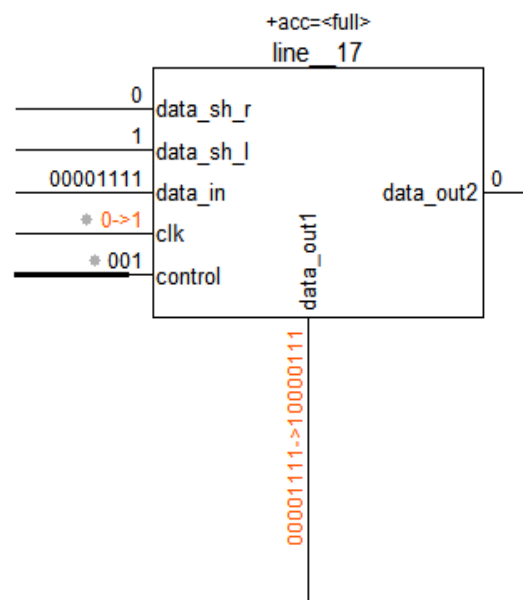

Shift right with 1




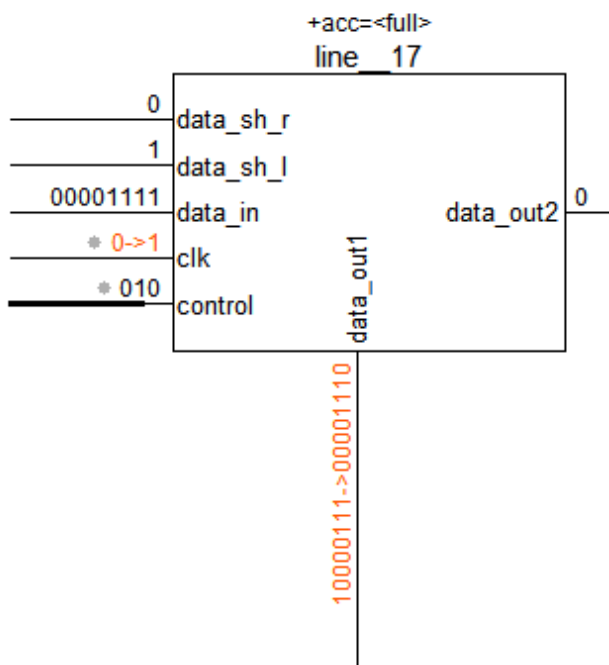


Shift left with 0

 

Rotate right

SUPER REGISTER

 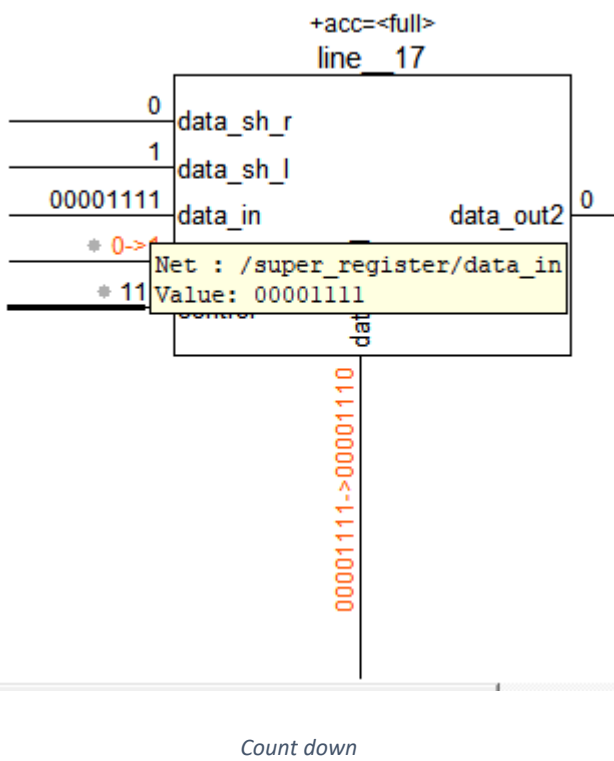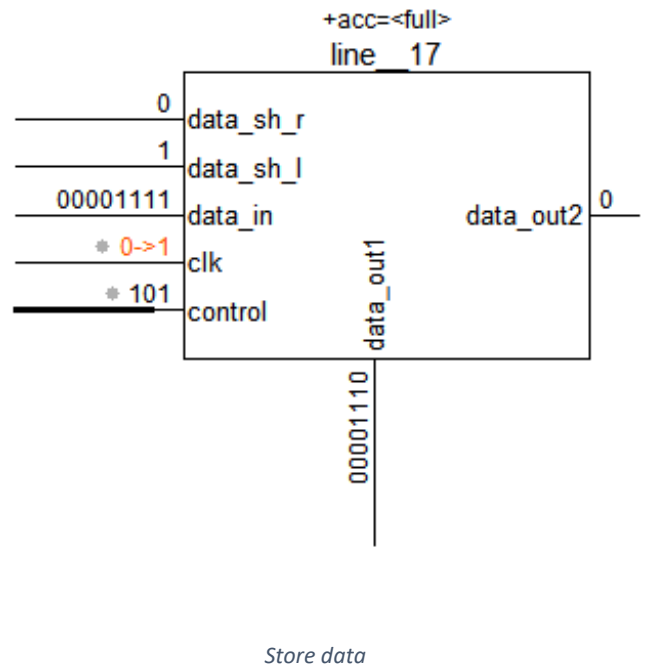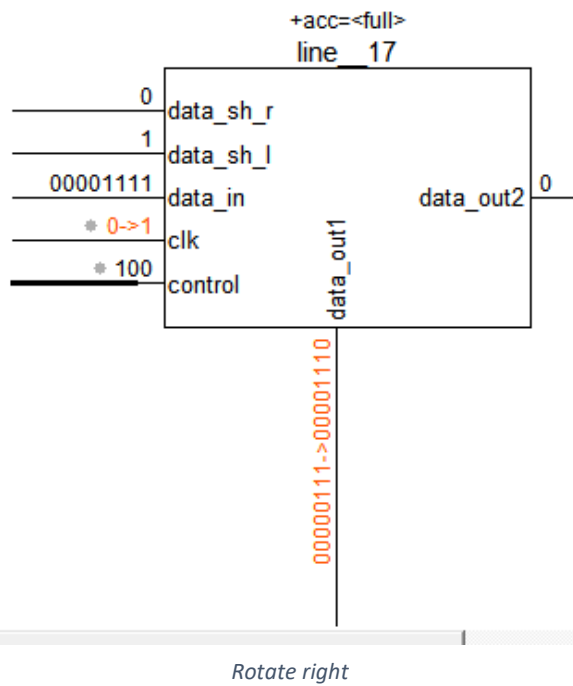

SUPER REGISTER

[illegible]